



System on Chip Design Lab.  
晶片系統設計實驗室

# Chapter 4 - part I

## Datapath and Control Single-cycle

**Tien-Fu Chen**

Dept. of Computer Science  
**National Chiao Tung Univ.**

Material source:  
COD RISC-V slides


# Chap 4 overview

---

- ❑ CPU performance factors
  - Instruction count: Determined by ISA and compiler
  - CPI and Cycle time: Determined by CPU hardware
- ❑ We will examine two RISC-V implementations
  - **Chap 4-part1**: A simplified RISC-V
    - Datapath & control
  - **Chap 4-part2**: A more realistic pipelined version
    - Datapath & control
  - **Chap 4-part3**: Advanced pipelined design
- ❑ Simple subset, shows most aspects
  - Memory reference: l d, sd
  - Arithmetic/logical: add, sub, and, or
  - Control transfer: beq
 
# Recap Logic Design Basics


- ❑ Information encoded in binary
  - Low voltage = 0, High voltage = 1
  - One wire per bit
  - Multi-bit data encoded on multi-wire buses
- ❑ Combinational element
  - Operate on data
  - Output is a function of input
- ❑ State (sequential) elements
  - Store information



# Combinational Elements


- AND-gate

$$Y = A \& B$$

 


- Multiplexer

$$Y = S ? I_1 : I_0$$

 


- Adder

$$Y = A + B$$

 


- Arithmetic/Logic Unit

$$Y = F(A, B)$$

 


 
# Clocking Methodology

- ❑ Combinational logic transforms data during clock cycles
  - Between clock edges
  - Input from state elements, output to state element
  - Longest delay determines clock period



 
 
# Sequential Elements

- ❑ Register: stores data in a circuit
  - Uses a clock signal to determine when to update the stored value
  - Edge-triggered: update when Clk changes from 0 to 1


  
# Sequential Elements

- ❑ Register with write control
  - Only updates on clock edge when write control input is 1
  - Used when stored value is required later






**Let us start a simple  
RISC-V datapath**




# Basic components for Datapath



## □ Instruction Fetch

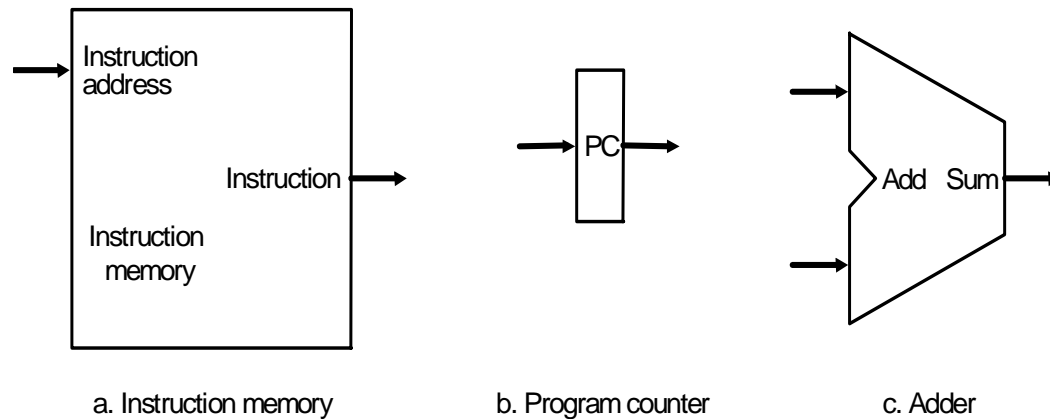


## □ Memory and sign extension

 






## □ datapath for R-type instructions

 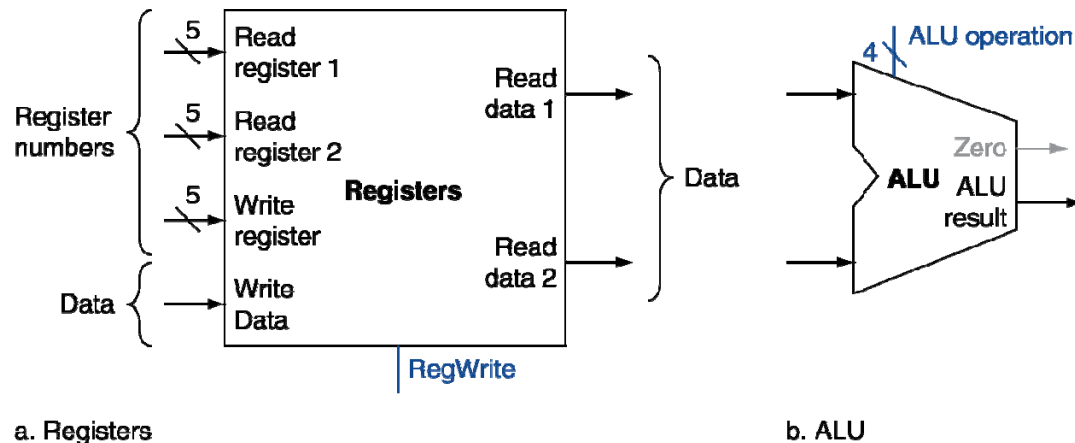

# Instruction Fetch

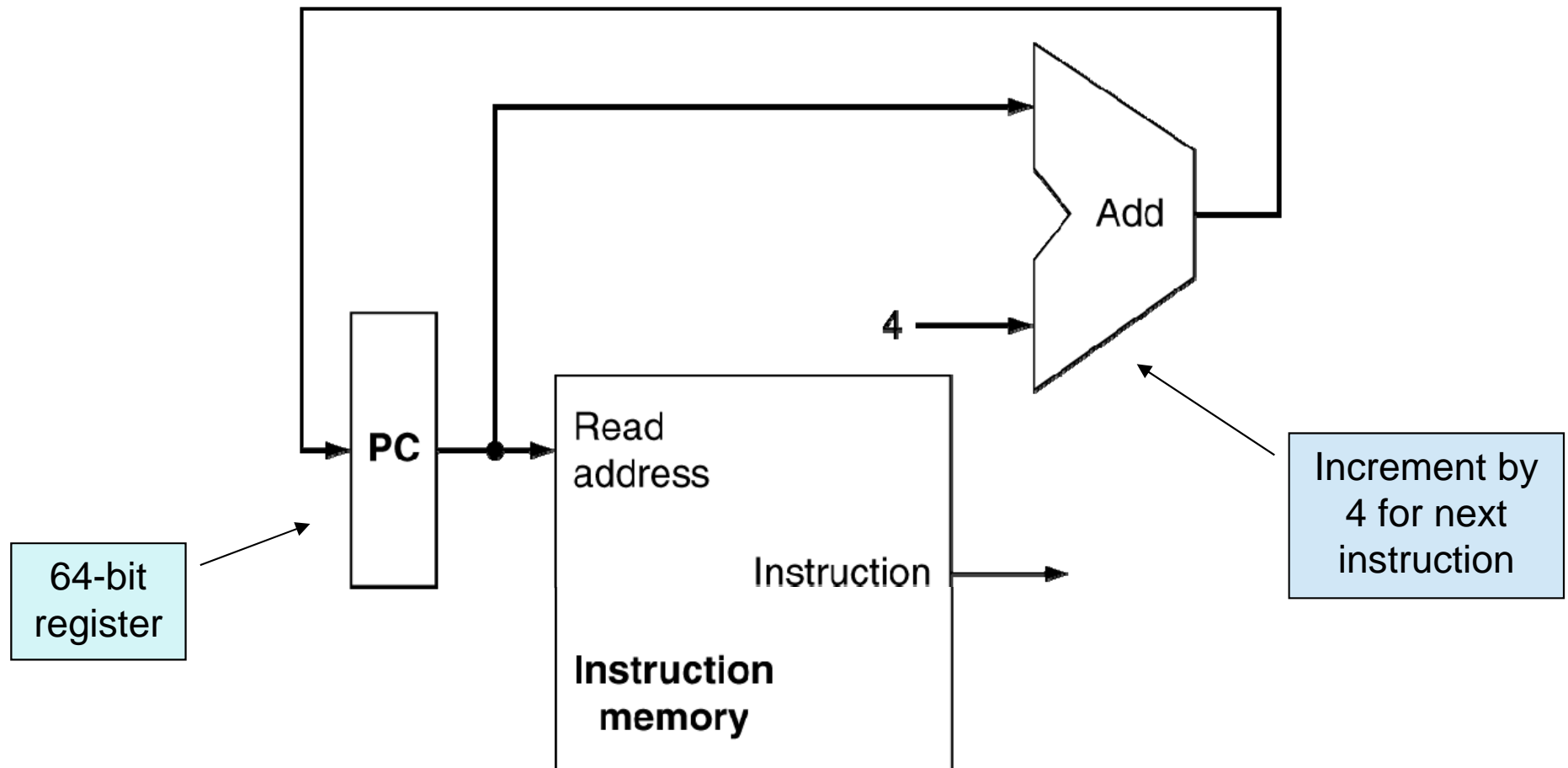


# A Quick building up??

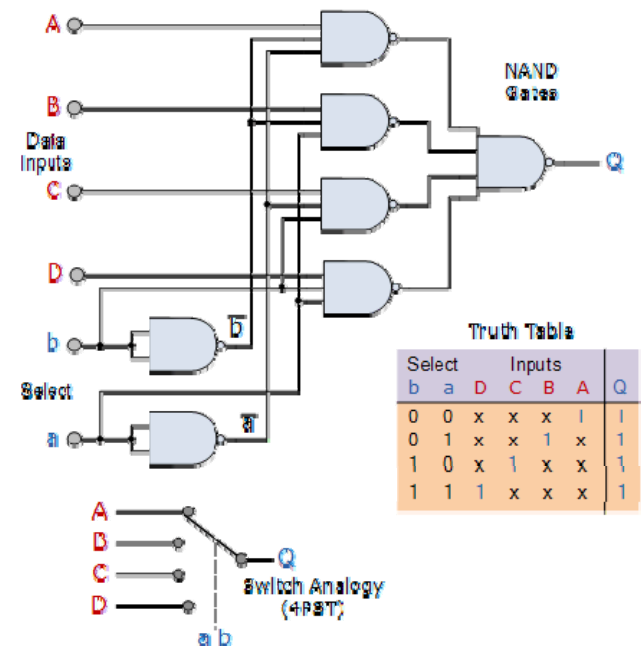  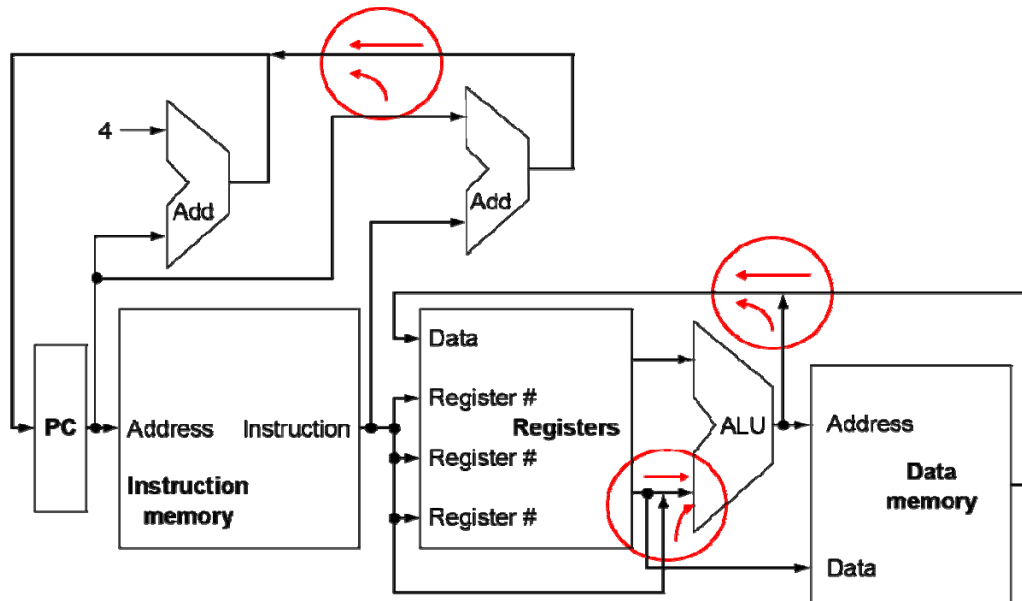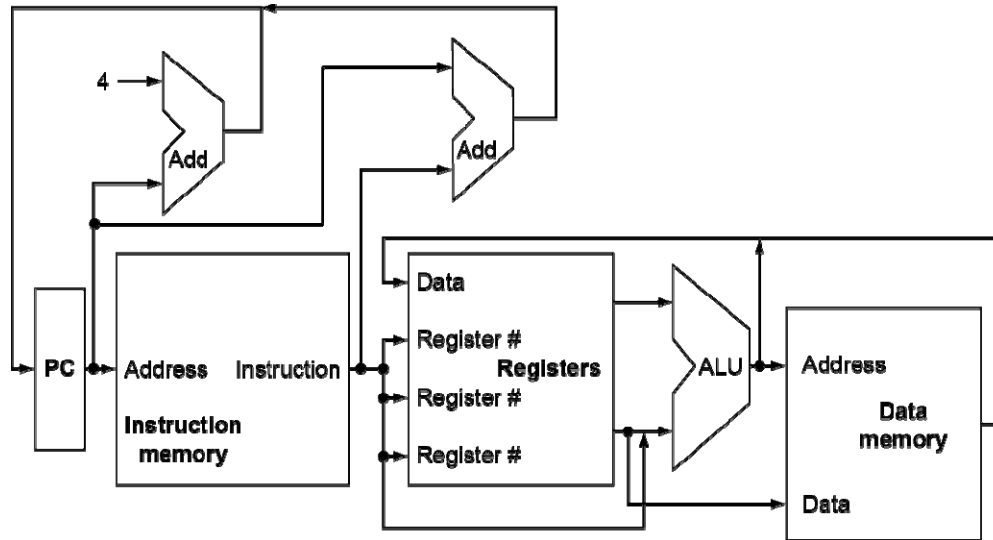

# R-type: add instruction



□ add x9,x20,x21

funct7	rs2	rs1	funct3	rd	opcode
7 bits	5 bits	5 bits	3 bits	5 bits	7 bits
0	21	20	0	9	51

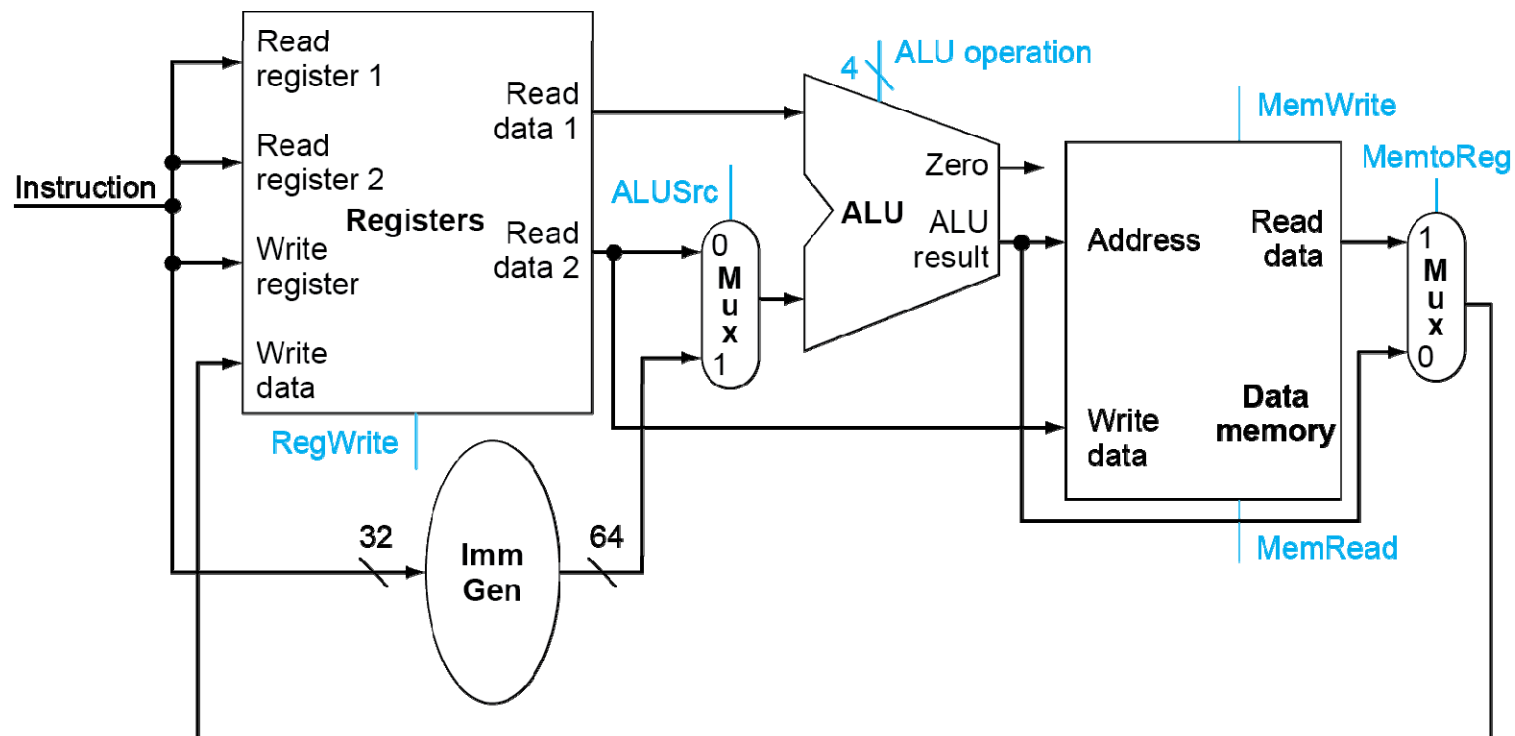




# I-Format: load instruction

lw x14, 8(x2)

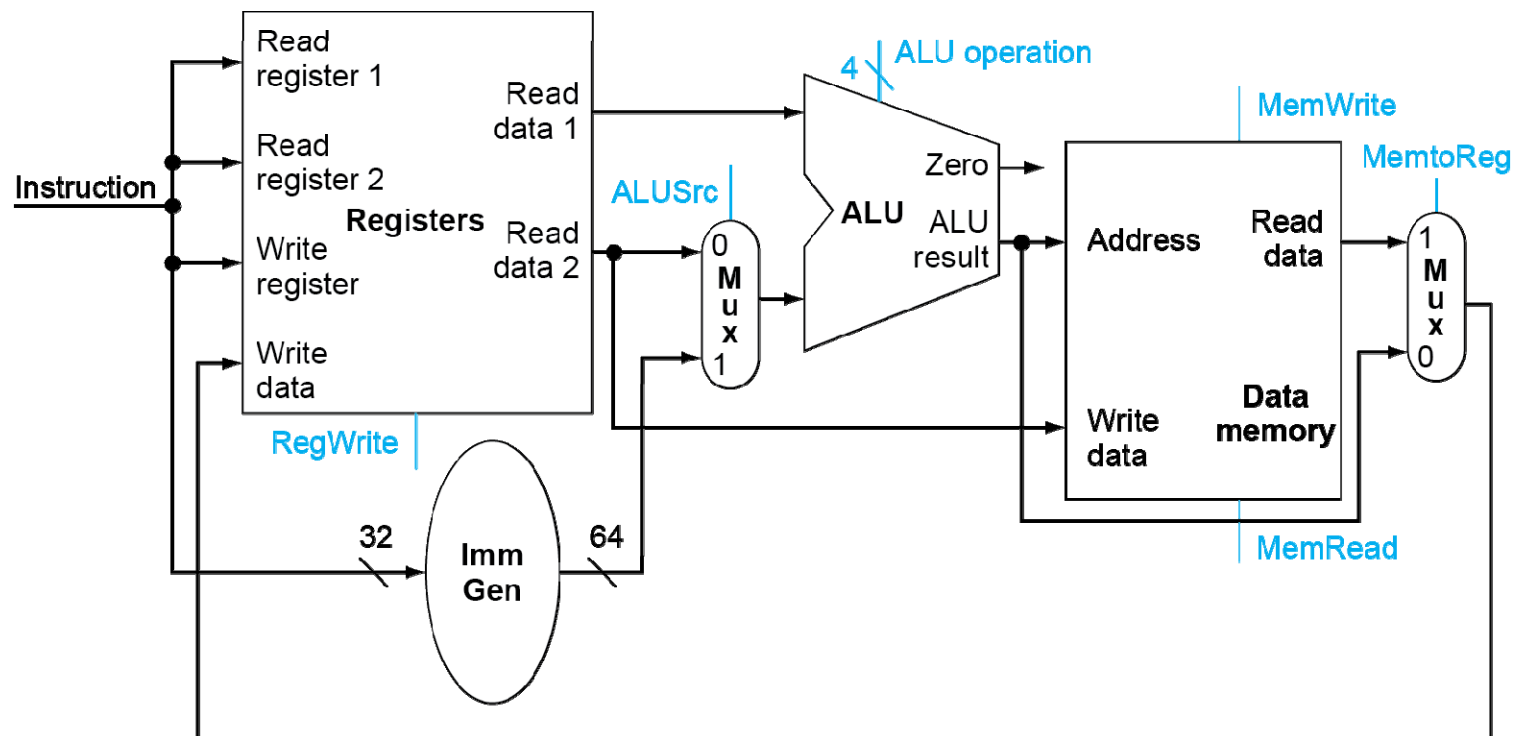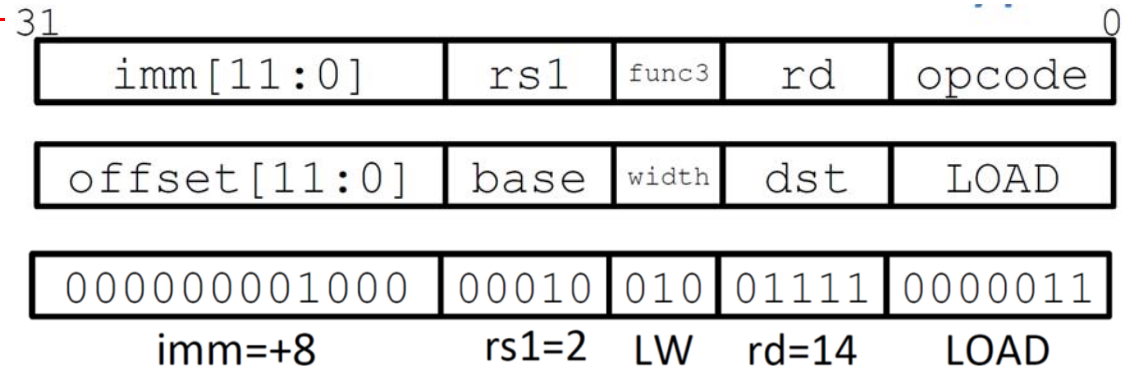

# S-Format: store instruction

**sw x14, 8(x2)**

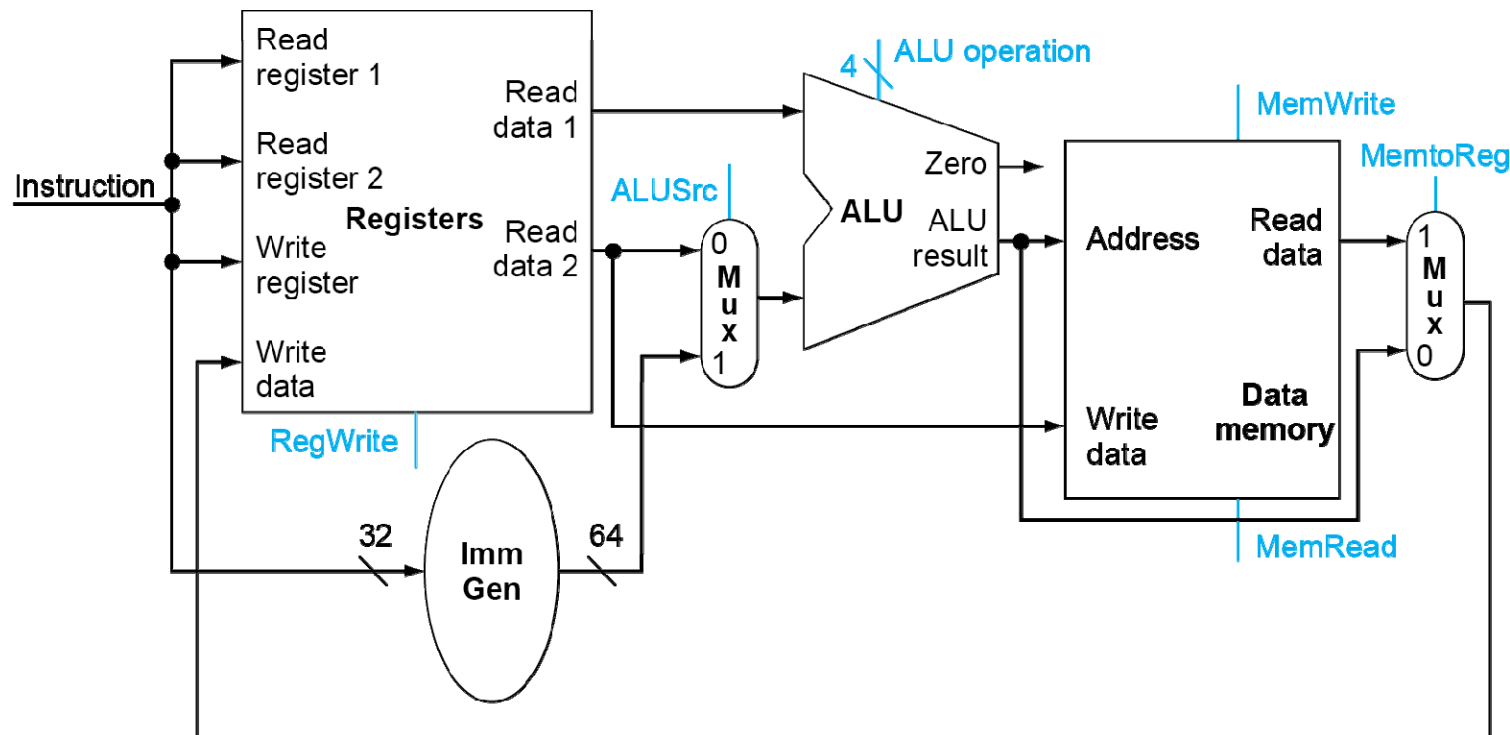 
 



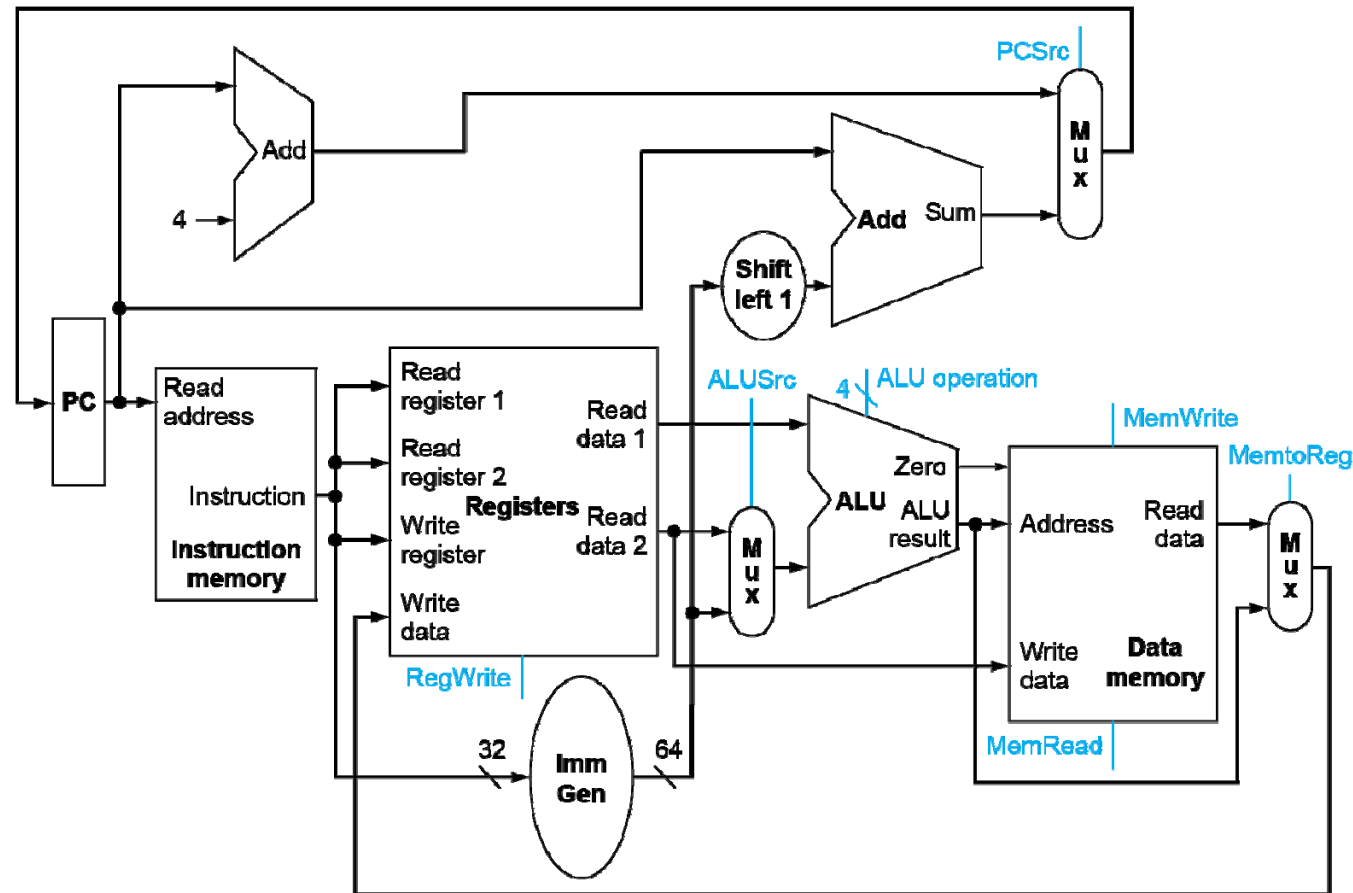 
# Branch instructions –

❑ beq x19,x10,End


- mem[PC]
- if ((R[rs] - R[rt]) eq 0)  
 $PC \leftarrow PC + \text{sign-extend}(\text{imm13})$   
 else  
 $PC \leftarrow PC + 4$






# Observations between MIPS and RISC-v

# MIPS

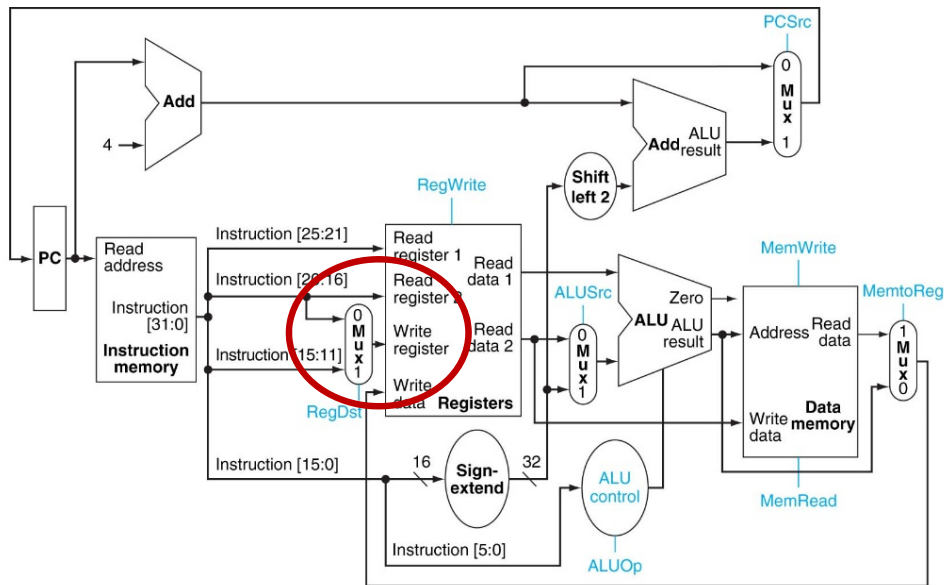

# RISC-V

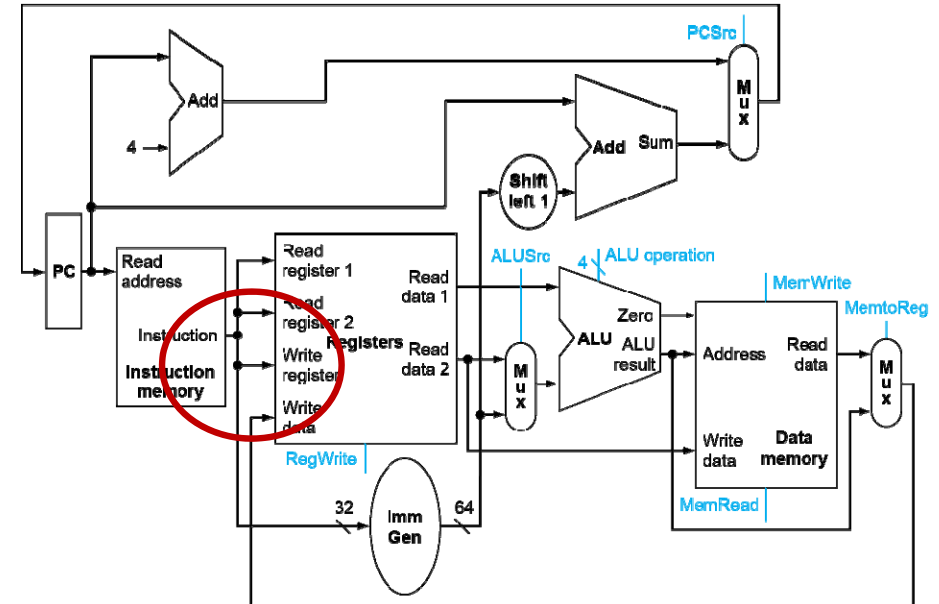

Name	Fields						Comments
Field size	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits	All MIPS instructions are 32 bits long
R-format	op	rs	rt	rd	shamt	funct	Arithmetic instruction format
I-format	op	rs	rt	address/immediate			Transfer, branch, i mm. format
J-format	op	target address					Jump instruction format

Name (Field Size)	Field					Comments	
	7 bits	5 bits	5 bits	3 bits	5 bits		7 bits
R-type	funct7	rs2	rs1	funct3	rd	opcode	Arithmetic instruction format
I-type	immediate[11:0]		rs1	funct3	rd	opcode	Loads & Immediate arithmetic
S-type	immed[11:5]	rs2	rs1	funct3	immed[4:0]	opcode	Stores
SB-type	immed[12:10:5]	rs2	rs1	funct3	immed[4:1,1,1]	opcode	Conditional branch format
UJ-type	immediate[20,10:1,11,10:12]				rd	opcode	Unconditional jump format
U-type	immediate[31:12]				rd	opcode	Upper Immediate format

## Good design of instruction set architecture does matter!!



**Let us add control  
to simple RISC-V**


# Control

- ❑ Information comes from the 32 bits of the instruction
  - Determine control signals from 6-bit opcode field
- ❑ Selecting the operations to perform (ALU, read/write, etc.)
- ❑ Controlling the flow of data (multiplexor inputs)
  - **ALUsrc**
  - **MemtoReg**
- ❑ Enable/Disable control signals
  - **Branch, MemRead, MemWrite, RegWrite**
- ❑ ALU's operation based on instruction type and function code
  - **ALUop**

# ALU Control

- ❑ ALU used for
    - Load/Store: F = add
    - Branch: F = subtract
    - R-type: F depends on opcode
- Don't confuse with add or sub instructions

ALU control	Function
0000	AND
0001	OR
0010	add
0110	subtract

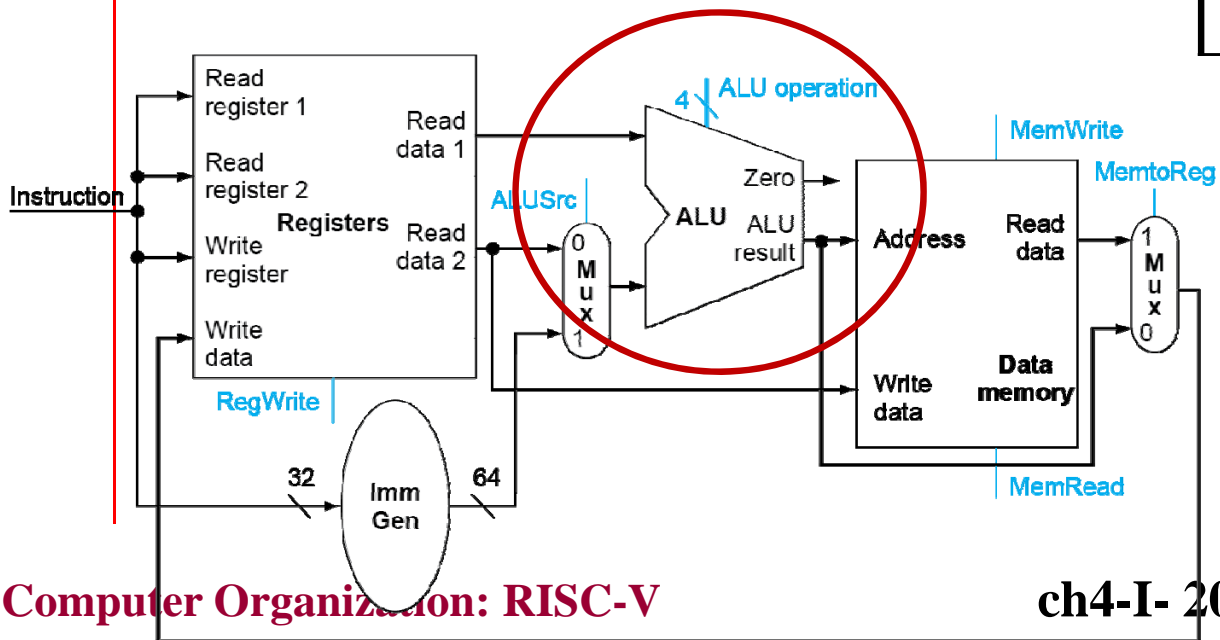



# Determine ALU control

## □ ALU control input

0000 AND  
0001 OR  
0010 add  
0110 subtract  
0111 set-on-less-than  
1100 NOR
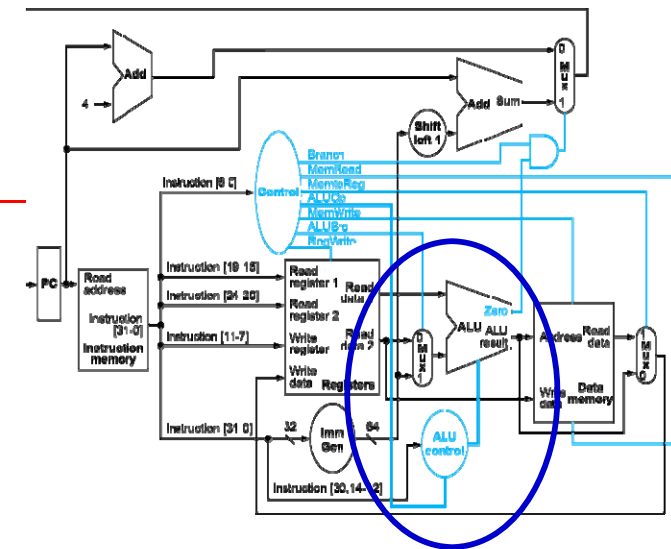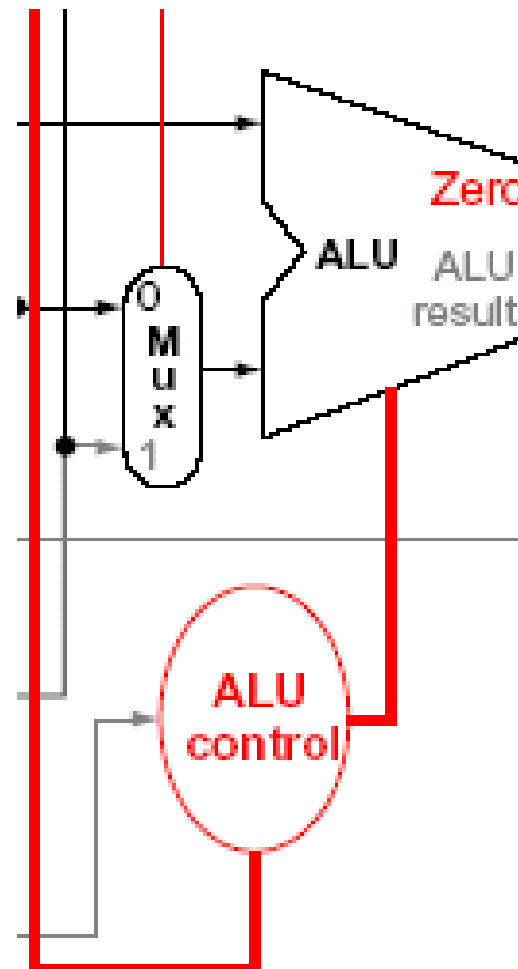
## □ Using ALUOP to indicate instruction type

00 = lw, sw  
01 = beq,  
1x = arithmetic




# ALU Control

- ❑ Assume 2-bit ALUOp derived from opcode
  - Combinational logic derives ALU control


opcode	ALUOp	Operation	Opcode field	ALU function	ALU control
ld	00	load register	XXXXXXXXXXXX	add	0010
sd	00	store register	XXXXXXXXXXXX	add	0010
beq	01	branch on equal	XXXXXXXXXXXX	subtract	0110
R-type	10	add	100000	add	0010
		subtract	100010	subtract	0110
		AND	100100	AND	0000
		OR	100101	OR	0001
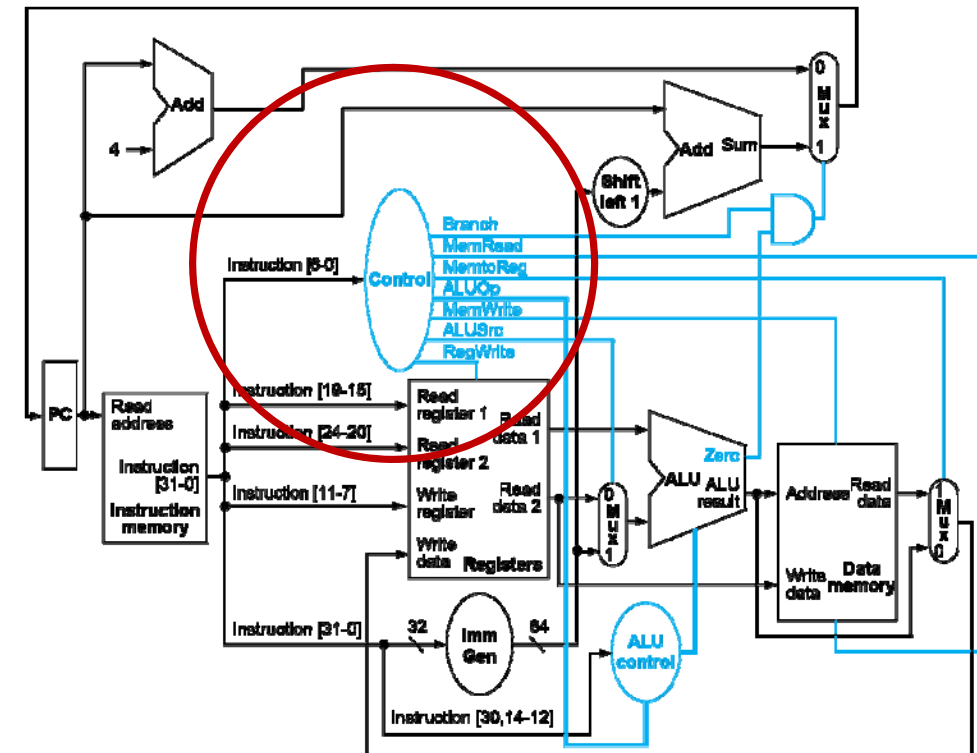
# Control function specified by truth table



Input or output	Signal name	R-format	ld	sd	beq
Inputs	I[6]	0	0	0	1
	I[5]	1	0	1	1
	I[4]	1	0	0	0
	I[3]	0	0	0	0
	I[2]	0	0	0	0
	I[1]	1	1	1	1
	I[0]	1	1	1	1
Outputs	ALUSrc	0	1	1	0
	MemtoReg	0	1	X	X
	RegWrite	1	1	0	0
	MemRead	0	1	0	0
	MemWrite	0	0	1	0
	Branch	0	0	0	1
	ALUOp1	1	0	0	0
	ALUOp0	0	0	0	1

# Main control

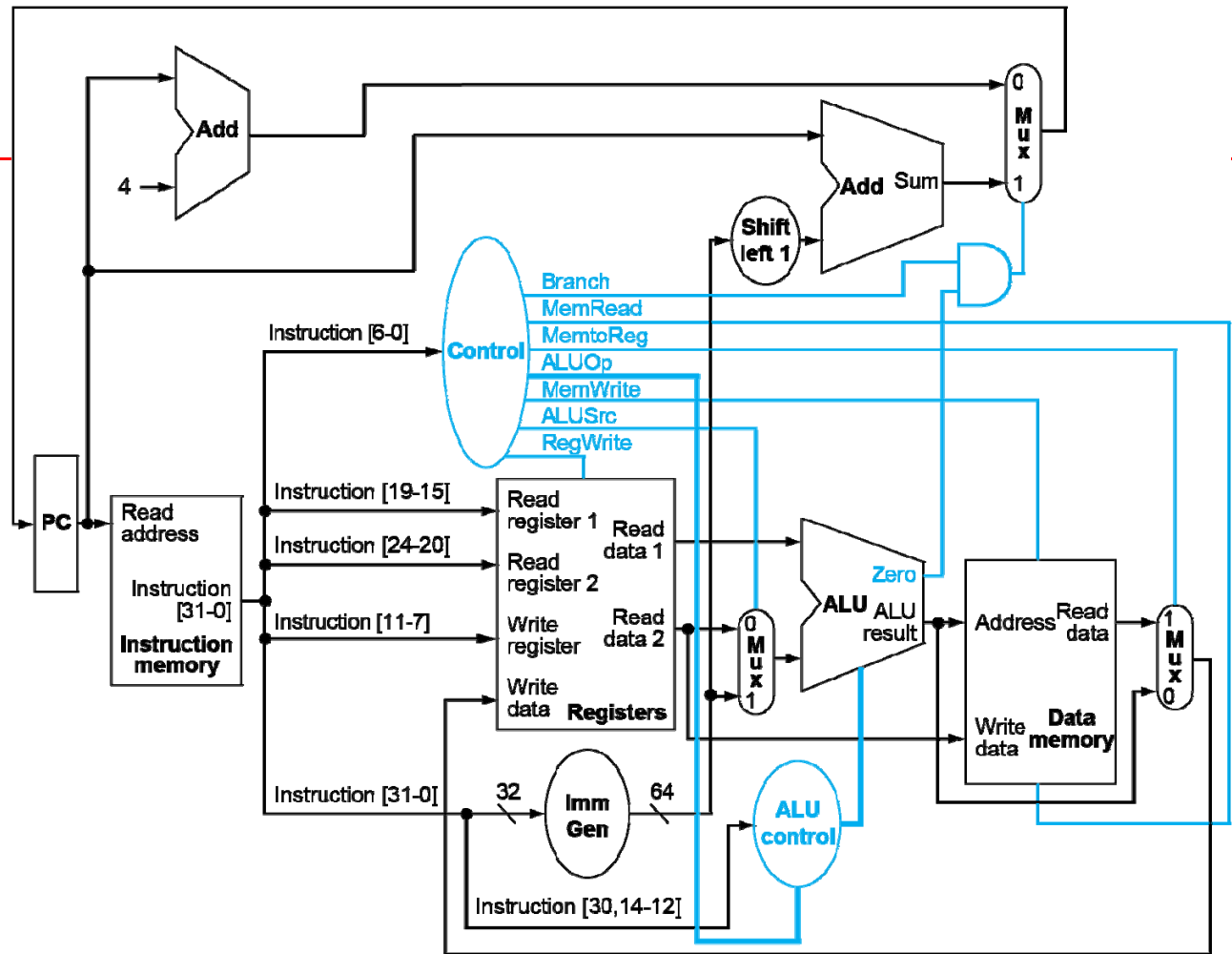

Instruction	RegDst	ALUSrc	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALU Op0
R-format								
lw								
sw								
beq								



# The Main Control Unit


- Control signals derived from instruction

Name (Bit position)	Fields					
	31:25	24:20	19:15	14:12	11:7	6:0
(a) R-type	funct7	rs2	rs1	funct3	rd	opcode
(b) I-type	immediate[11:0]		rs1	funct3	rd	opcode
(c) S-type	immed[11:5]	rs2	rs1	funct3	immed[4:0]	opcode
(d) SB-type	immed[12,10:5]	rs2	rs1	funct3	immed[4:1,11]	opcode


ALUOp		Funct7 field							Funct3 field			Operation
ALUOp1	ALUOp0	I[31]	I[30]	I[29]	I[28]	I[27]	I[26]	I[25]	I[14]	I[13]	I[12]	
0	0	X	X	X	X	X	X	X	X	X	X	0010
X	1	X	X	X	X	X	X	X	X	X	X	0110
1	X	0	0	0	0	0	0	0	0	0	0	0010
1	X	0	1	0	0	0	0	0	0	0	0	0110
1	X	0	0	0	0	0	0	0	1	1	1	0000
1	X	0	0	0	0	0	0	0	1	1	0	0001

# Control for ALU

Name (Bit position)	Fields				
	31:25	24:20	19:15	14:12	11:7
(a) R-type	funct7	rs2	rs1	funct3	rd
(b) I-type	immediate[11:0]		rs1	funct3	rd
(c) S-type	immed[11:5]	rs2	rs1	funct3	immed[4:0]
(d) SB-type	immed[12,10:5]	rs2	rs1	funct3	immed[4:1,11]

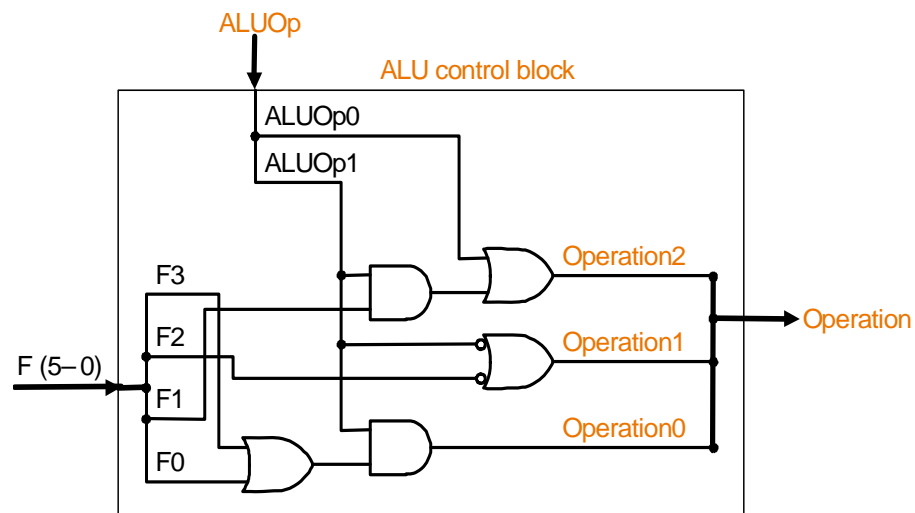

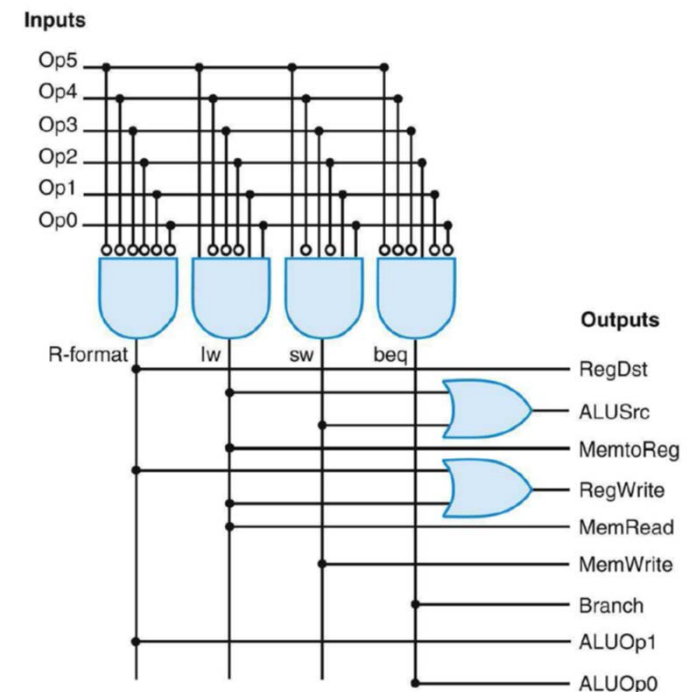- Generate control logic using a truth table (can turn into gates):



- Implemented by programmable logic array (PLA)

# Performance of Single-cycle Machine

- ❑ Calculate cycle time assuming negligible delays except:
  - memory (200ps), ALU and adders (100ps), register file access (100ps)

Inst. class	Inst mem	Reg read	ALU operatn	Data mem	Reg write	total
R-type						
LW						
SW						
branch						
Jump						

- ❑ Cycle time

# Real encoding

31	25	24	20	19	15	14	12	11	7	6	0	
funct7			rs2	rs1		funct3		rd	opcode			R-type
0000000			rs2	rs1		000		rd	0110011			ADD
0100000			rs2	rs1		000		rd	0110011			SUB
0000000			rs2	rs1		001		rd	0110011			SLL
0000000			rs2	rs1		010		rd	0110011			SLT
0000000			rs2	rs1		011		rd	0110011			SLTU
0000000			rs2	rs1		100		rd	0110011			XOR
0000000			rs2	rs1		101		rd	0110011			SRL
0100000			rs2	rs1		101		rd	0110011			SRA
0000000			rs2	rs1		110		rd	0110011			OR
0000000			rs2	rs1		111		rd	0110011			AND

Reg-Reg Instruction

32-bit R-type ALU

31	20	19	15	14	12	11	7	6	0	
imm[11:0]		rs1		funct3		rd		opcode		I-type
imm[11:0]		rs1		000		rd		0000011		LB
imm[11:0]		rs1		001		rd		0000011		LH
imm[11:0]		rs1		010		rd		0000011		LW
imm[11:0]		rs1		100		rd		0000011		LBU
imm[11:0]		rs1		101		rd		0000011		LHU

load instruction

31	25	24	20	19	15	14	12	11	7	6	0		
imm[11:5]			rs2		rs1		funct3		imm[4:0]		opcode		S-type
imm[11:5]			rs2		rs1		000		imm[4:0]		0100011		SB
imm[11:5]			rs2		rs1		001		imm[4:0]		0100011		SH
imm[11:5]			rs2		rs1		010		imm[4:0]		0100011		SW

store instruction