
 




ld x14, 8(x2)

Load-1

 



ld x14, 8(x2)

Load-2

  



ld x14, 8(x2)

Load-3

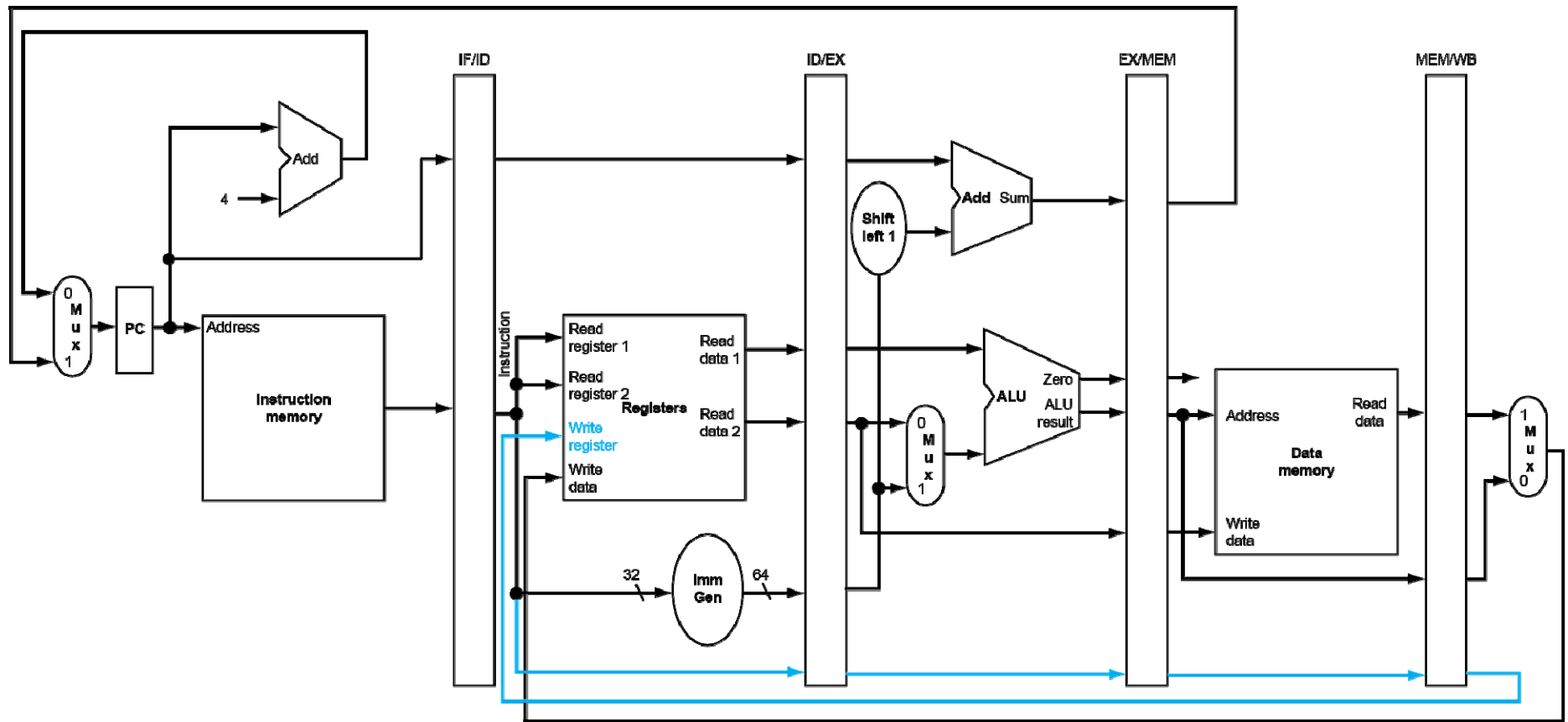 



ld x14, 8(x2)


Load-4

  

ld x14, 8(x2)

Load-5

  


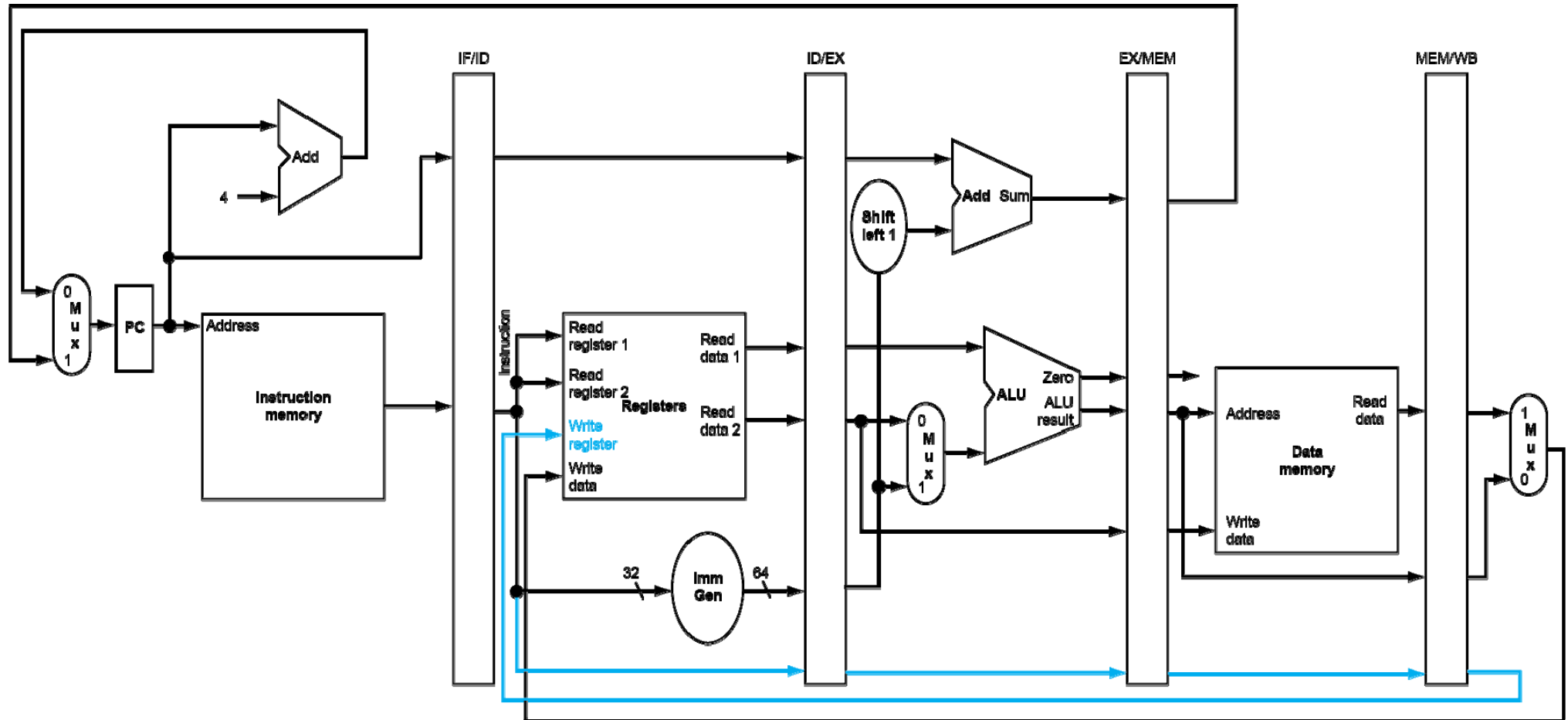

```

add    x4, x1,x3
lw     x12,30(x2)
sw     x13,50(x6)
beq    x14,x2,100


```

 

```

add    x4, x1,x3
lw     x12,30(x2)
sw     x13,50(x6)
beq    x14,x2,100


```

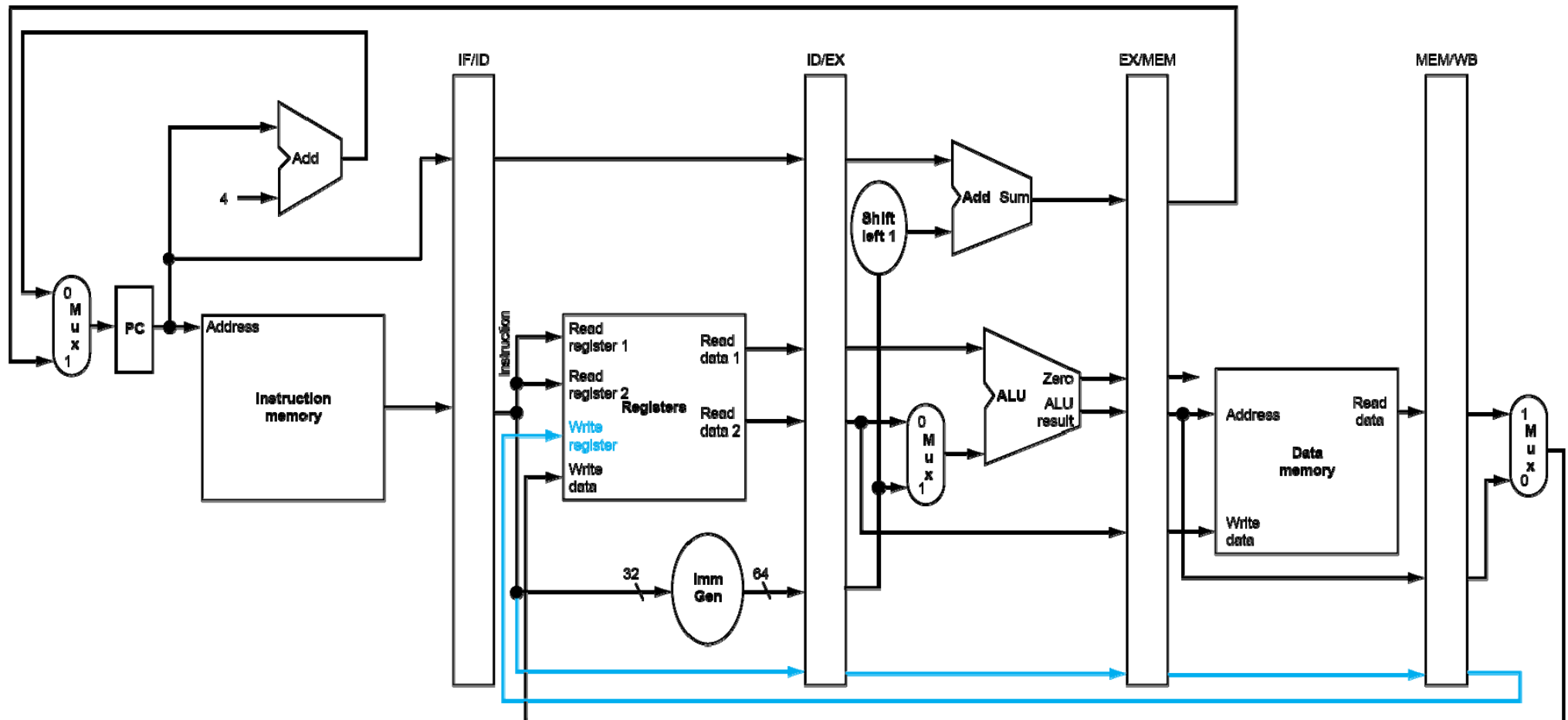

```

add    x4, x1,x3
lw     x12,30(x2)
sw     x13,50(x6)
beq    x14,x2,100


```
 
```

add    x4, x1,x3
lw     x12,30(x2)
sw     x13,50(x6)
beq    x14,x2,100


```

 

```

add    x4, x1, x3
lw     x12, 30(x2)
sw     x13, 50(x6)
beq    x14, x2, 100


```

 

```

add    x4, x1,x3
lw     x12,30(x2)
sw     x13,50(x6)
beq    x14,x2,100

```

 


```

add    x4, x1, x3
lw     x12, 30(x2)
sw     x13, 50(x6)
beq    x14, x2, 100

```


Instruction	Execution/Address Calculation stage control lines				Memory access stage control lines			Write-back stage control lines	
	Reg Dst	ALU Op1	ALU Op0		Branch	Mem Read	Mem Write	Reg write	Mem to Reg
R-format									
lw									
sw									
beq									

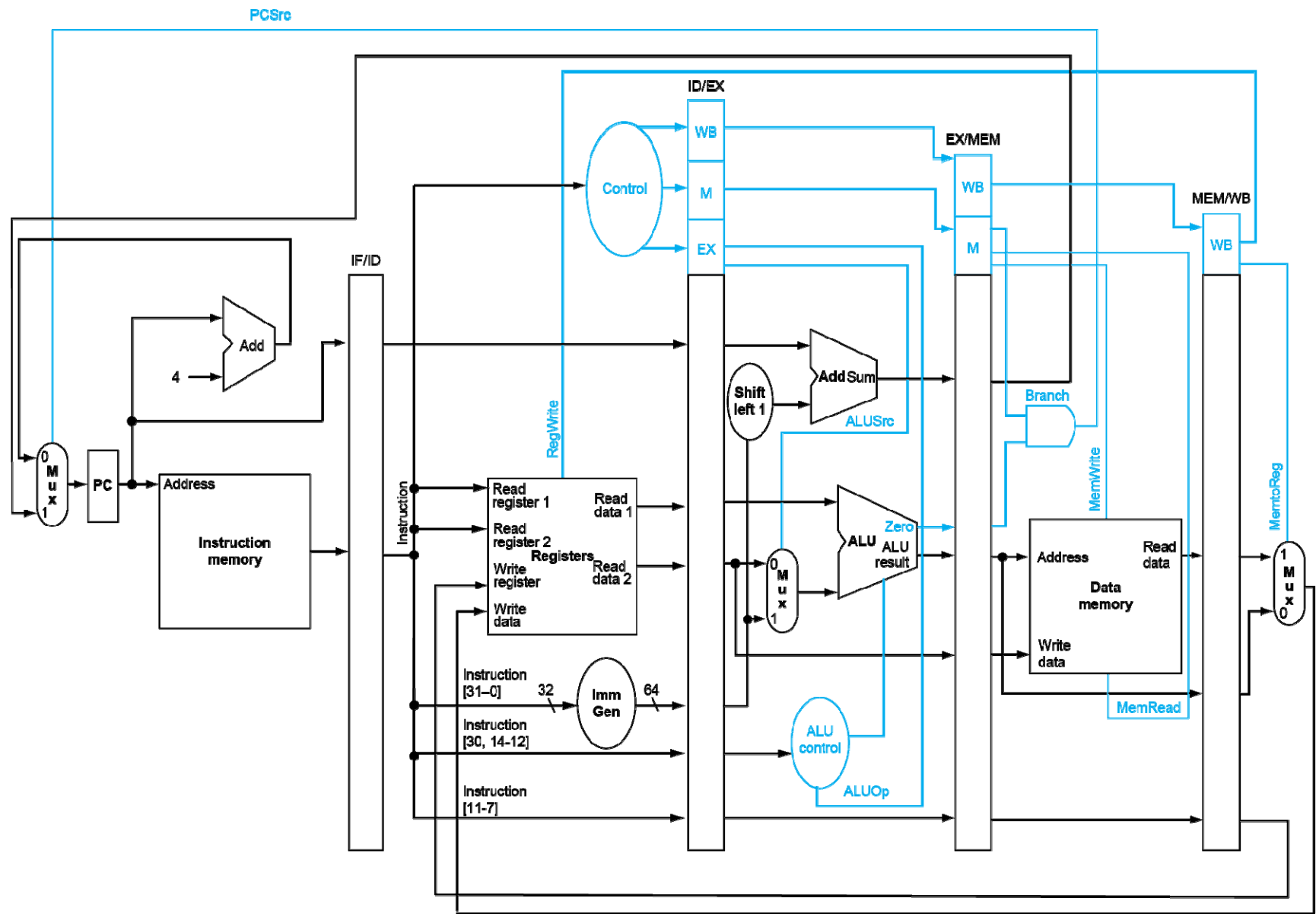
add x4, x1,x3
lw x12,30(x2)
sw x13,50(x6)
beq x14,x2,100




Instruction	Execution/Address Calculation stage control lines				Memory access stage control lines			Write-back stage control lines	
	Reg Dst	ALU Op1	ALU Op0		Branch	Mem Read	Mem Write	Reg write	Mem to Reg
R-format									
lw									
sw									
beq									

 add x4, x1,x3
lw x12,30(x2)
sw x13,50(x6)
beq x14,x2,100



 [illegible]


```
add    x4, x1,x3
lw     x12,30(x2)
sw     x13,50(x6)
beq    x14,x2,100
```

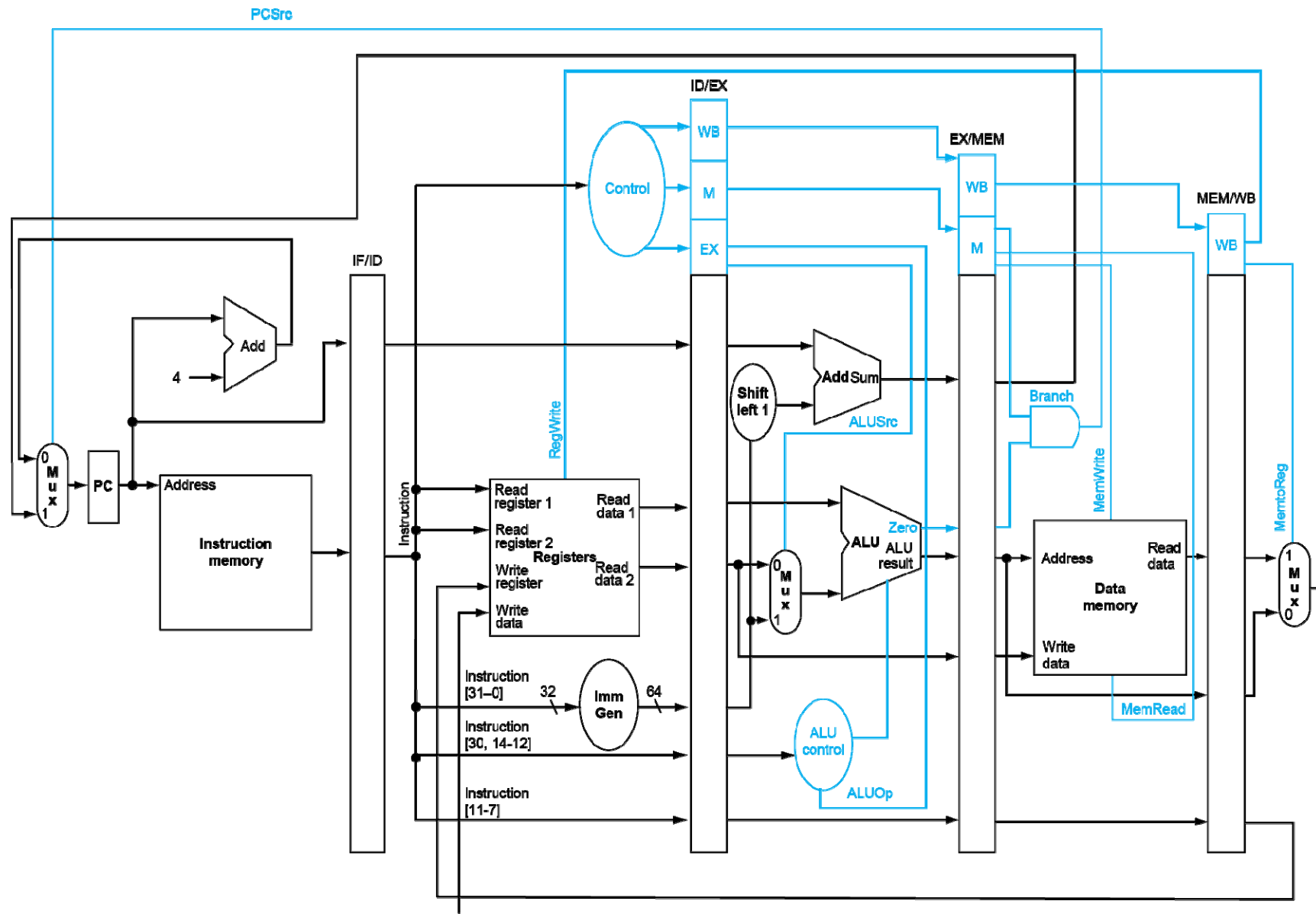
[illegible]

```
add    x4, x1,x3
lw     x12,30(x2)
sw     x13,50(x6)
beq    x14,x2,100
```



Instruction	Execution/Address Calculation stage control lines				Memory access stage control lines			Write-back stage control lines	
	Reg Dst	ALU Op1	ALU Op0		Branch	Mem Read	Mem Write	Reg write	Mem to Reg
R-format									
lw									
sw									
beq									

 add x4, x1,x3
lw x12,30(x2)
sw x13,50(x6)
beq x14,x2,100




  


sub x2, x1,x3
and x12,x2,x5
or x13,x6,x2
add x14,x2,x2
sw x15,100(x2)



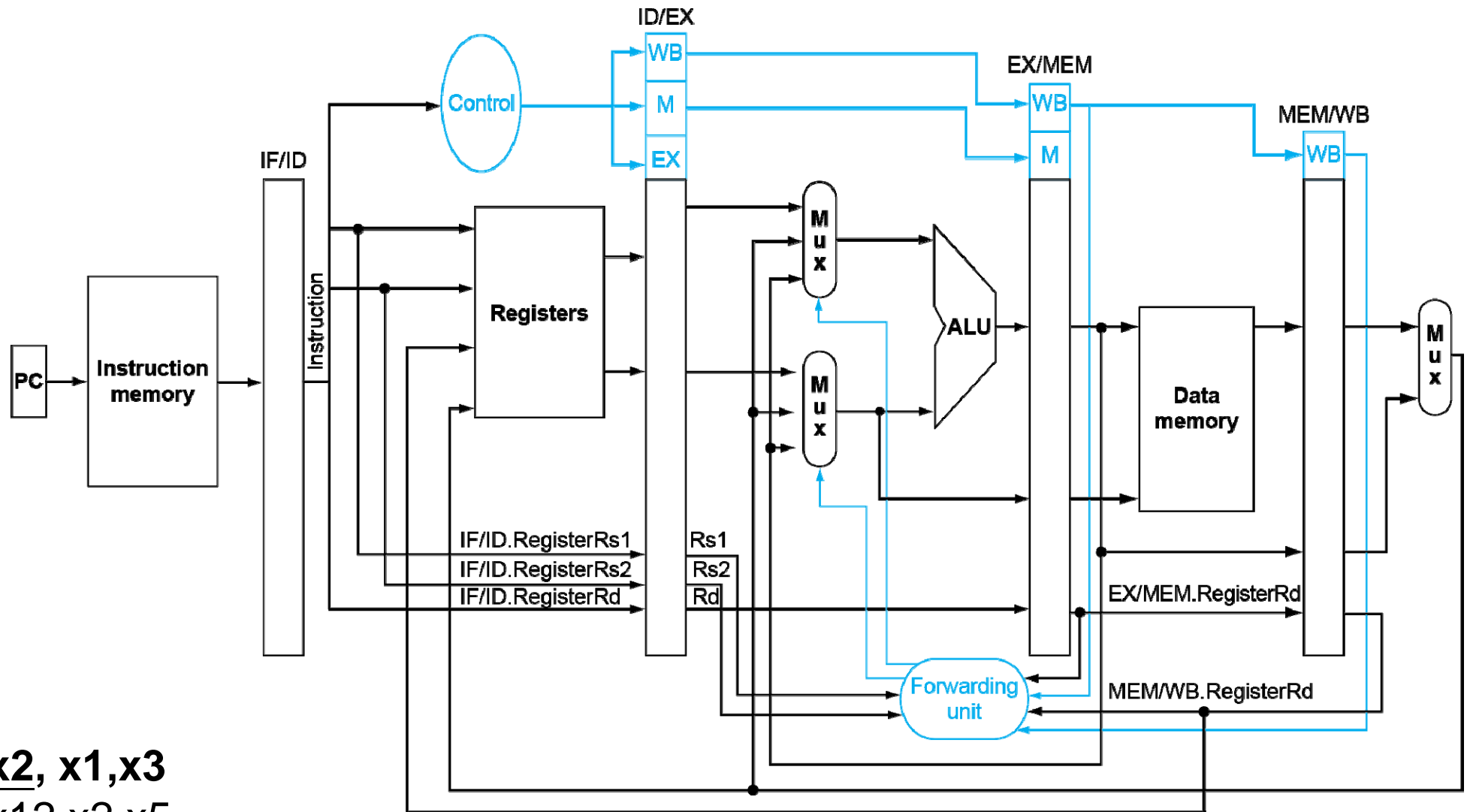
sub x2, x1,x3
and x12,x2,x5
or x13,x6,x2
add x14,x2,x2
sw x15,100(x2)



 
sub x2, x1,x3
and x12,x2,x5
or x13,x6,x2
add x14,x2,x2
sw x15,100(x2)



 
sub x2, x1,x3
and x2,x2,x5
or x13,x6,x2
add x14,x2,x2
sw x15,100(x2)



 
sub x2, x1,x3
and x2,x2,x5
or x13,x6,x2
add x14,x2,x2
sw x15,100(x2)



 
sub x2, x1, x3
and x2, x2, x5
or x13, x6, x2
add x14, x2, x2
sw x15, 100(x2)



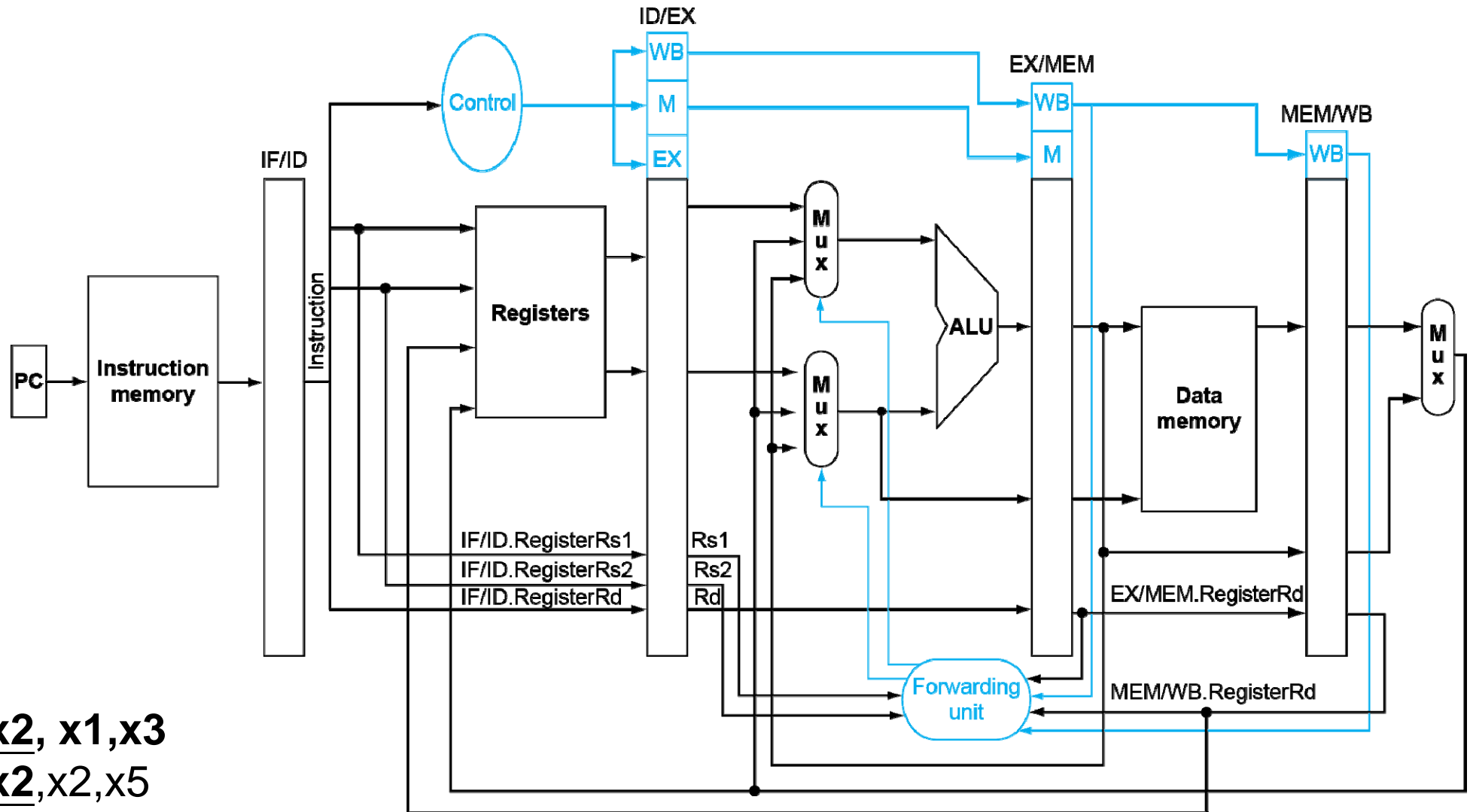
sub x2, x1,x3
and x2,x2,x5
or x13,x6,x2
add x14,x2,x2
sw x15,100(x2)



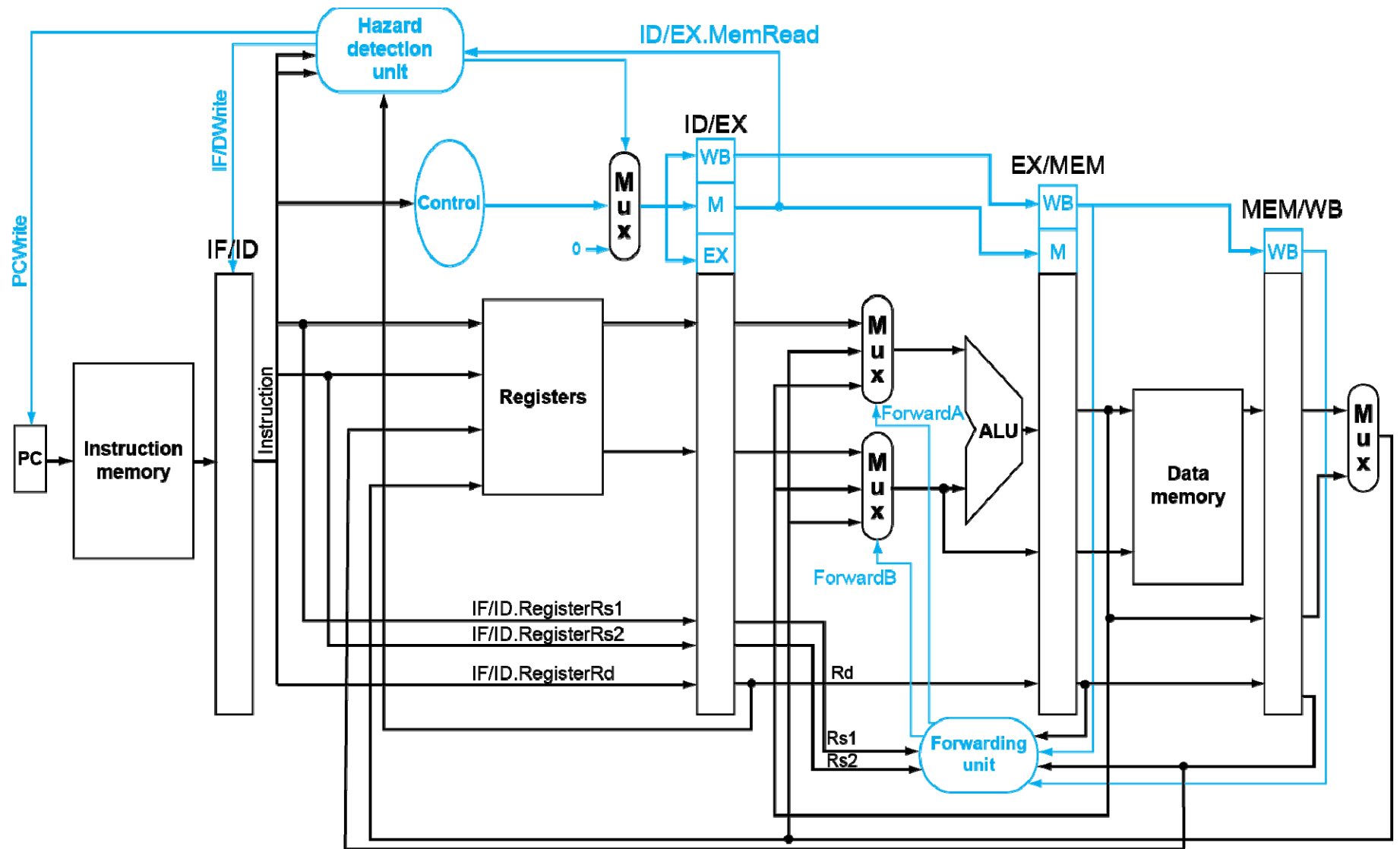
sub x2, x1, x3
and x2, x2, x5
or x13, x6, x2
add x14, x2, x2
sw x15, 100(x2)



 
lw **x2,30(x3)**
 and x4,x2,x5
 or x13,x6,x4
 add x14,x8,x9



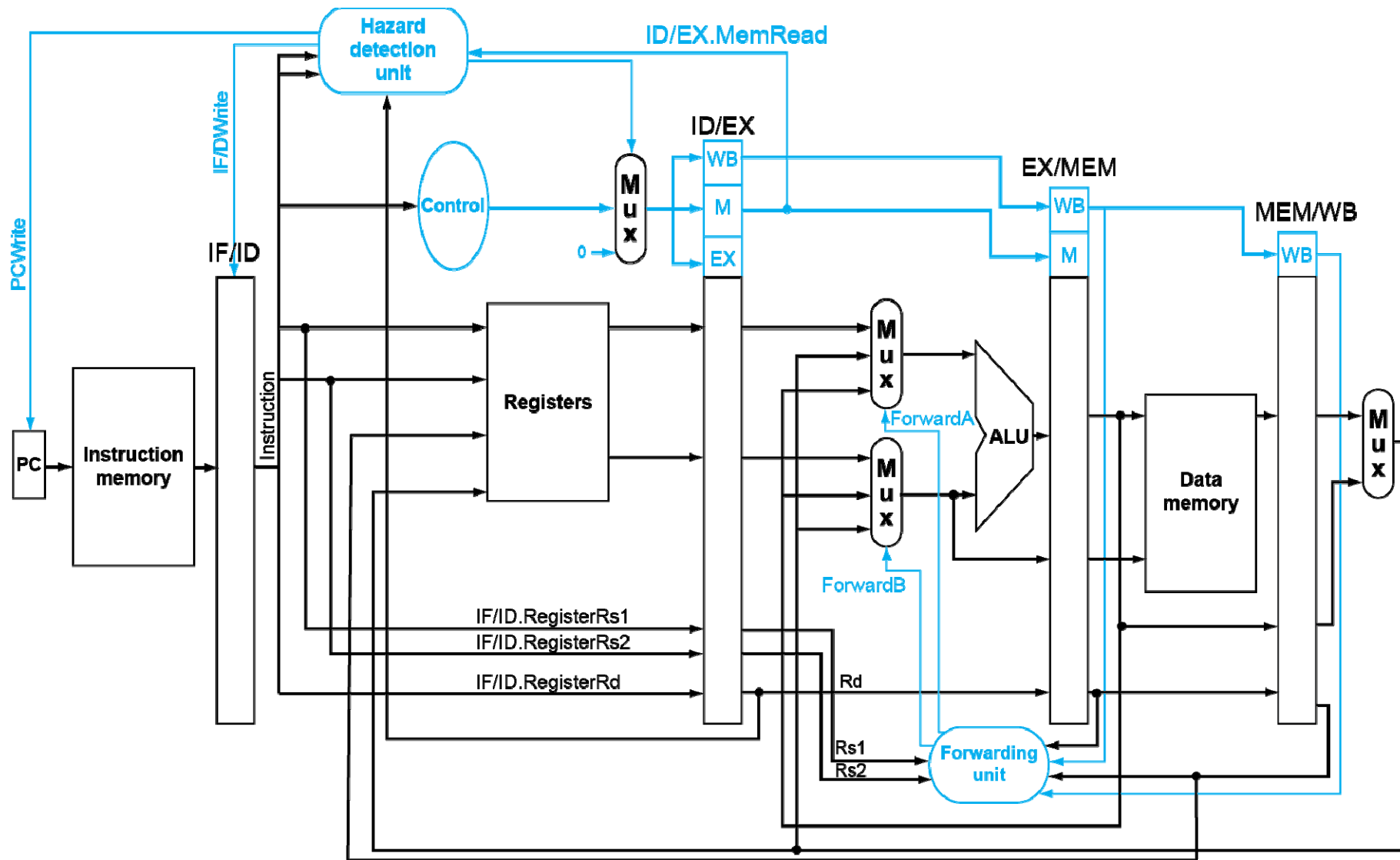
lw x2,30(x3)
and x4,x2,x5
or x13,x6,x4
add x14,x8,x9



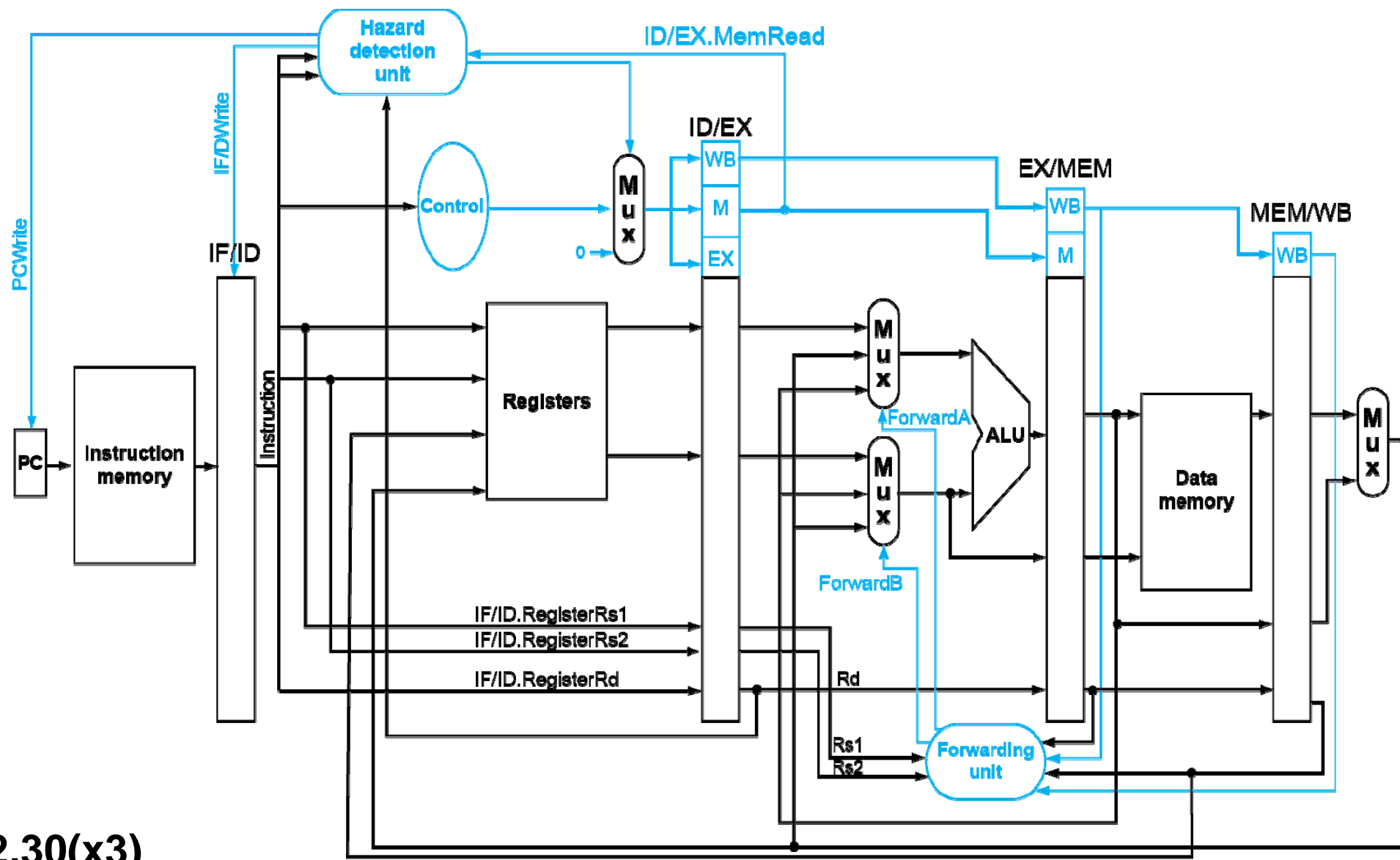
lw x2,30(x3)
and x4,x2,x5
or x13,x6,x4
add x14,x8,x9



 lw x2,30(x3)
and x2,x2,x5
or x13,x6,x2
add x14,x8,x9



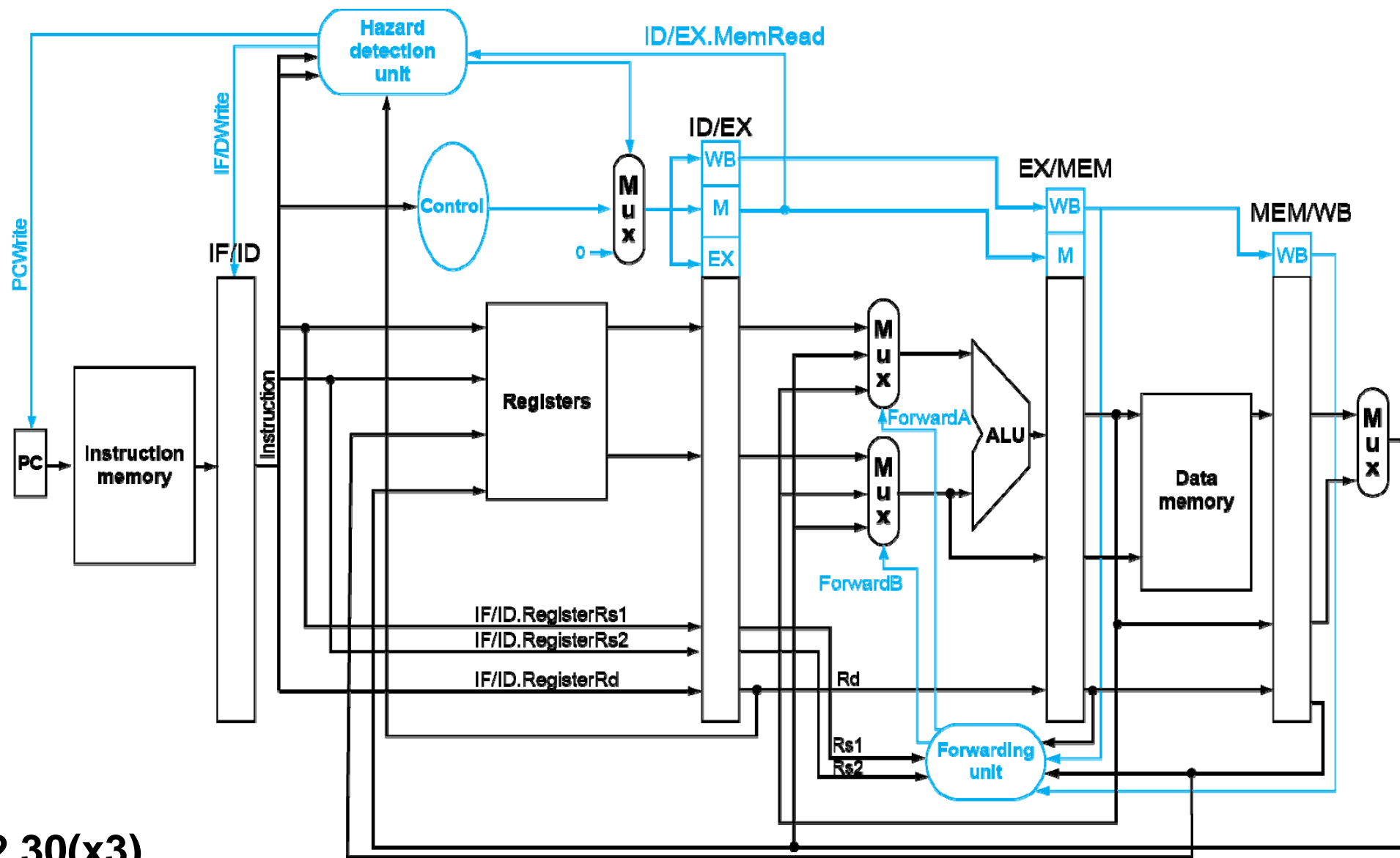lw x2,30(x3)
and x2,x2,x5
or x13,x6,x2
add x14,x8,x9



lw x2,30(x3)
and x2,x2,x5
or x13,x6,x2
add x14,x8,x9