

Computer Organization, Spring 2019

Lab 1: 32-bit ALU

Due: 2019/4/15

1. Goal

The goal of this LAB is to implement a 32-bit ALU (Arithmetic Logic Unit) with 32 1-bit ALUs. ALU is the basic computing component of a CPU. Its operations include AND, OR, addition, subtraction, etc. This series of LABs will help you understand the CPU architecture.

2. HW Requirement

- (1) Please use **Icarus Verilog** and **GTKWave** as your HDL simulator.
- (2) Please attach **your name** and **student ID** as comment at the top of each file.
- (3) Please use the Testbench we provide you, and DO NOT modify it.
- (4) The names of top module and IO ports must be named as follows:

Top module: alu.v

```
module alu(
    rst_n,          // negative reset          (input)
    src1,           // 32 bits source 1          (input)
    src2,           // 32 bits source 2          (input)
    ALU_control,    // 4 bits ALU control input  (input)
    result,         // 32 bits result            (output)
    zero,           // 1 bit when the output is 0, zero must be set (output)
    cout,           // 1 bit carry out           (output)
    overflow        // 1 bit overflow            (output)
);
```

ALU starts to work when the signal rst_n is 1, and then catches the data from src1 and src2.

In order to have a good coding style, please obey the rules below:

One module is written in one file.

Module name and file name must be the same.

For example: The file "alu.v" only contains the module "alu".


- (5) Basic instruction set (60%)

ALU action	Description	ALU control input
AND	Bitwise and	0000
OR	Bitwise or	0001
ADD	Addition (with overflow)	0010
SUB	Subtract	0110
NOR	Bitwise nor	1100
NAND	Bitwise nand	1101
SLT	Set less than (signed)	0111

(6) ZCV three flags: zero, carry out, and overflow (30%)

Flag name	Operation
Zero	Output 1 when the output of ALU is 0 Otherwise, output 0
Cout	Output 1 when the carry-out is 1 (for ADD SUB) Otherwise, output 0
Overflow	Output 1 when signed overflow happens (for ADD SUB) Otherwise, output 0


3. Architecture diagram

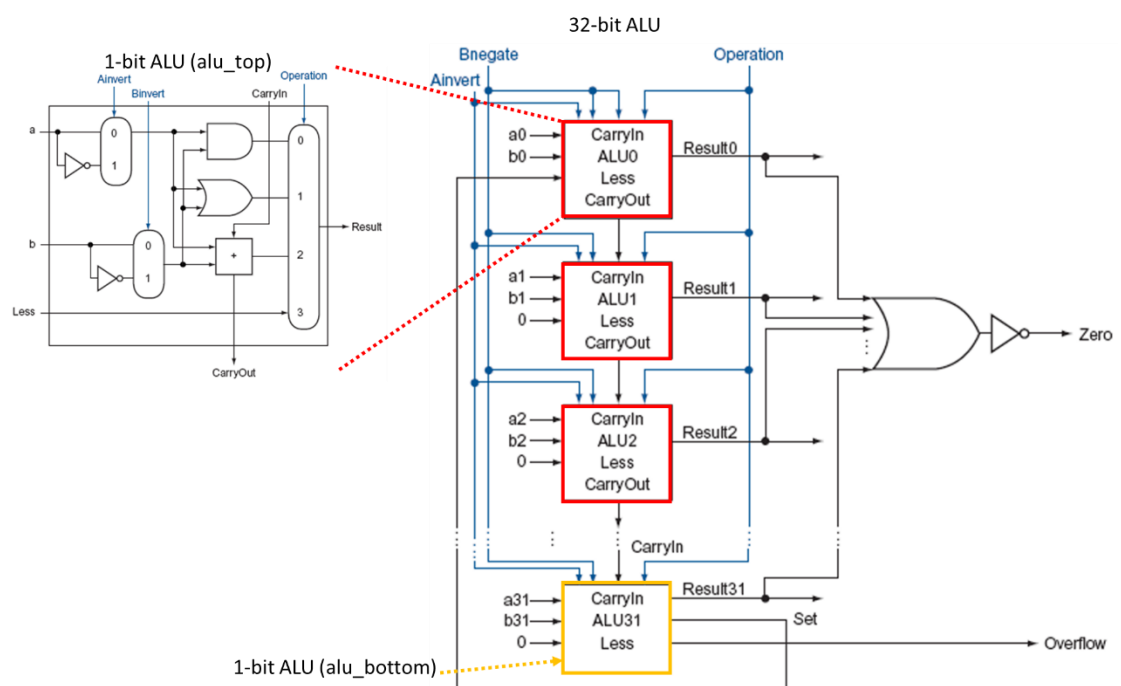

4. Bonus: Extra instruction set (10%)

ALU action	Description	ALU control input
SLT	Set less than	0111_000
SGT	Set greater than	0111_001
SLE	Set less equal	0111_010
SGE	Set greater equal	0111_011
SEQ	Set equal	0111_110
SNE	Set not equal	0111_100

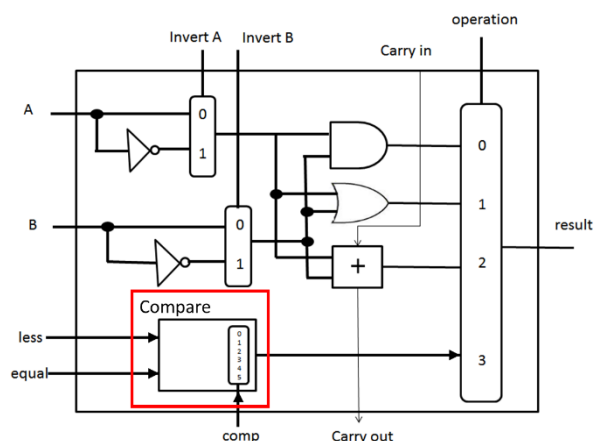Hint: Add a module named “Compare” in 1-bit ALU!



5. Report (10%)

Please hand in a **PDF** file with the following contents:

- (1) Your architecture diagram
- (2) Detailed description of the implementation
- (3) Command for compiling your source codes
 - If you have implemented the bonus part, leave a command as:
`iverilog -o bonus.vvp testbench.v <source code 1> ... <source code N>`
 - If you have implemented only the basic part, leave a command as:
`iverilog -o basic.vvp testbench.v <source code 1> ... <source code N>`
- (4) Problems encountered and solutions
- (5) Lesson learnt (if any)

6. Grade

- (1) Total: 110 points, including 10 points for your report
- (2) Late submission: 10 points off per day
- (3) **No plagiarism, or you will get 0 point.**

7. Hand in

- (1) Zip your folder and name it as "ID.zip" (e.g., 0616xxx.zip) before uploading to New e3. Other filenames and formats such as *.rar and *.7z are NOT accepted! Multiple submissions are accepted, and the version with the latest time stamp will be graded.
- (2) Please include ONLY Verilog source codes (*.v) and your report (0616xxx.pdf) in the zipped folder.

8. How to test

The function of testbench is to read input data automatically and output erroneous data. Please put all the .txt files and your program in the same folder, after simulation finishes, you will get some information.

```
*****
SEQ error!
No. 8 error!
Correct result: 00000001    Correct ZCV: 000
Your result: xxxxxxxx    Your ZCV: x00
*****
```

Partial error:

```
*****
Congratulation! All data are correct!
*****
```

Or all cases pass:

9. Q&A

For any questions regarding Lab 1, please contact Ning-Chi Huang (blackitty321@gmail.com).